

Lab₁

Ben Frazer*

January 20, 2022

Contents

1	General	1
1.1	links	1
2	Theory	1
2.1	Surge Impedance	1
2.2	Electrical Length	2
2.3	Open Circuit Transmission line Voltage distribution	2
2.4	Matched Impedance Transmission line Voltage Distribution	2
2.4.1	Reactive Power Consumption	2
3	Experiment	2
3.1	Line Parameters	2
3.2	Surge Impedance (Part a)	2
3.3	Electrical length (Part b)	3

1 General

1.1 links

- video recording
- lab1 desc

2 Theory

2.1 Surge Impedance

$$Z_0 = \sqrt{\frac{L}{C}} \quad (2.1)$$

Where L and C are the line capacitance and reactance. ¹

*2704250F@student.gla.ac.uk

¹since this is given as a fraction it doesn't matter weather this is given as a per unit length value or as a total value

2.2 Electrical Length

This is effectively a measure of the amount of wavelengths of a particular frequency fit into a length of conductor. Electrical length is given by Equation 2.2.

$$\theta = \omega\sqrt{LC} \quad (2.2)$$

A value of $\theta = 2\pi$ would imply a single wavelength, however even for very long lines, typically values are $\ll 2\pi$.

2.3 Open Circuit Transmission line Voltage distribution

Voltage distribution along the line is given by Equation 2.3:

$$V(x) = V_s \frac{\cos(\theta(1 - x/a))}{\cos \theta} \quad (2.3)$$

Where x is defined as the distance from the sending end, a is the line length, and V_s is the phasor voltage at the sending end. setting $x = a$ and expression is derived for the voltage at the receiving end.

$$V_r = V(x = a) = \frac{V_s}{\cos \theta} \quad (2.4)$$

Since we assume that typical values of angle are $\ll 2\pi$ we know that as θ grows we expect V_r to increase from being exactly equal to V_s to a value $\geq V_s$

2.4 Matched Impedance Transmission line Voltage Distribution

The voltage profile for a line terminated in a matched impedance Z_0 would yield a perfectly flat voltage distribution i.e. $V(x) = V_s = V_r$. For any impedance greater than the surge impedance (Z_0) the voltage will tend to rise at the end of the transmission line while lower load impedance will cause the voltage profile in the line to sag leading to lower V_r .²

2.4.1 Reactive Power Consumption

When the load impedance is matched to the surge impedance ($Z_0 = Z_l$), the reactive power consumption of the line is zero. When $Z_l > Z_0$ the line generates reactive power whereas when $Z_l < Z_0$ the line consumes reactive power.

3 Experiment

3.1 Line Parameters

Line parameters are given by Table 3.1:

Table 3.1: *Per section model transmission line parameters*

$C_{\text{Sect}} (\mu \text{ F})$	$C_{\text{Tot}} (\mu \text{ F})$	$L_{\text{Sect}} (\text{mH})$	$L_{\text{tot}} (\text{mH})$	N_{Sections}	$f (\text{Hz})$	$\omega (\text{Rad/s})$
0.02	0.02	7.29	7.29	10	45.80307	287.78069

3.2 Surge Impedance (Part a)

Line surge impedance is calculated according to Equation 2.1 and the line parameters given in Table 3.1. Table shows the resulting surge impedance:

²this can be expressed also as higher voltage for loads lower than the surge load where $\text{surge load} \propto 1/Z_l$

Table 3.2: *Calculated Surge Impedance based on Equation 2.1 and Line Parameters in Table 3.1*

Surge impedance Z_0 (Ω)
1.6563467e-3

3.3 Electrical length (Part b)

Electrical length is calculated from Equation 2.2 and the line parameters given in Table 3.1